


Electronics
MSc. Physics Semester 2
Paper - MPHY CC-7
Unit 4
Topic – Half Adder and Full Adder

Dr. Surabhi Prasad
Prof.& Head
Department of Physics
Patna University

①

Half Adder

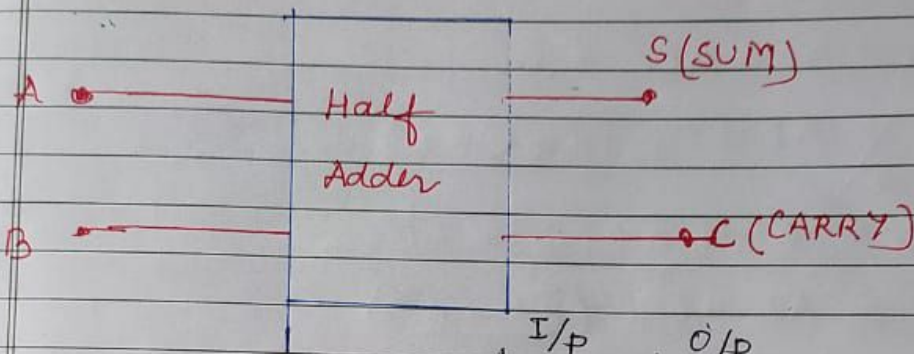A logic circuit for the addition of two one bit number is called Half Adder.




2^n
 $n = \text{no of input}$
 $2^2 = 4$

I/P		O/P	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

A \ B	0	1
0	0	1
1	1	0

$$S = AB\bar{B} + \bar{A}B = A \oplus B$$

$$C = AB$$

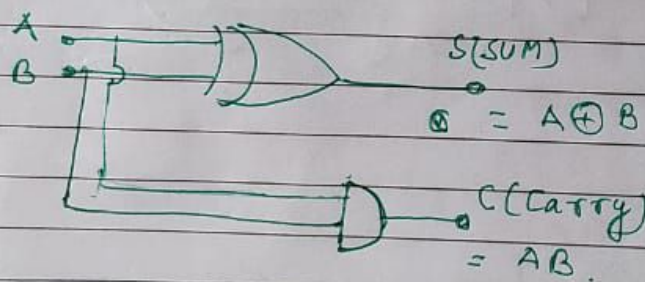

②

Full Adder

A full adder is a combinational circuit that adds two bits and carry and outputs a sum bit and a carry bit. It has two inputs and two outputs.



$$2^n = 2^3 = 8$$

A	B	C _{in}	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

K-map for S

		AB			
		00	01	11	10
C _{in}	0	0 ₀	1 ₂	0 ₅	1 ₄
	1	1 ₁	0 ₃	1 ₇	0 ₆

$$\begin{aligned}
 S &= \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + AB\bar{C}_{in} \\
 &\quad + A\bar{B}C_{in} \\
 &= \bar{A}\bar{B}C_{in} + AB\bar{C}_{in} \\
 &\quad + \bar{A}B\bar{C}_{in} + A\bar{B}C_{in}
 \end{aligned}$$

$$= (\bar{A}\bar{B} + AB)C_{in} +$$

$$+ (\bar{A}B + A\bar{B})\bar{C}_{in}$$

$$= (\bar{A} \oplus \bar{B})C_{in} + (A \oplus B)\bar{C}_{in}$$

$$= \bar{X}C_{in} + X\bar{C}_{in}$$

$$= \underbrace{X \oplus C_{in}} = \boxed{A \oplus B + C_{in}}$$

K-map for C

Cin	AB	00	01	11	10
0		0	0	1	0
1		0	1	1	1

$$C = AB + AC_{in} + BC_{in}$$


or,

$$C = AB + C_{in} (A \oplus B)$$

$$\begin{aligned} C &= AB + \bar{A}BC_{in} + ABC_{in} \\ &= AB + C_{in} (\bar{A}B + AB) \end{aligned}$$

$$C = AB + C_{in} (A \oplus B)$$

$$S = A \oplus B \oplus C_{in}$$



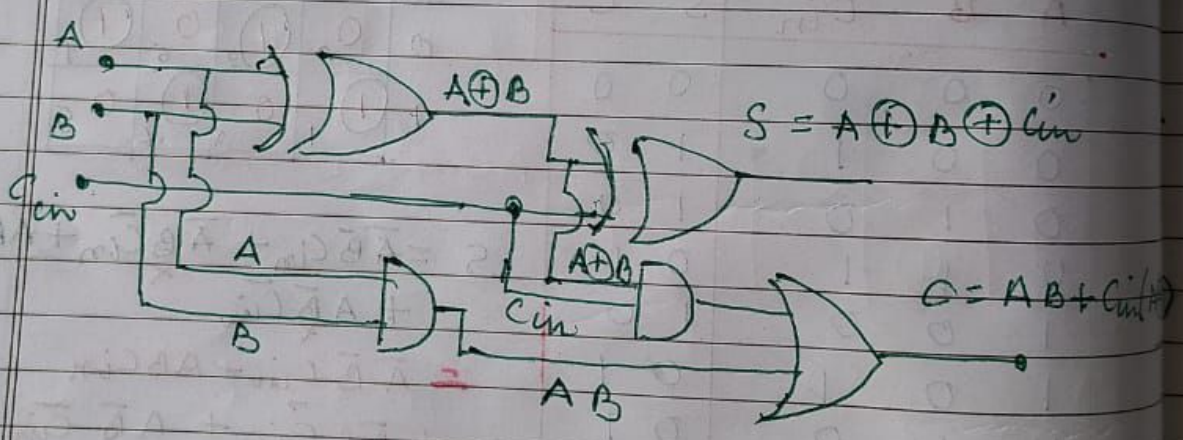


(4)

Full Adder Using Half Adder

Half Adder

Full Adder

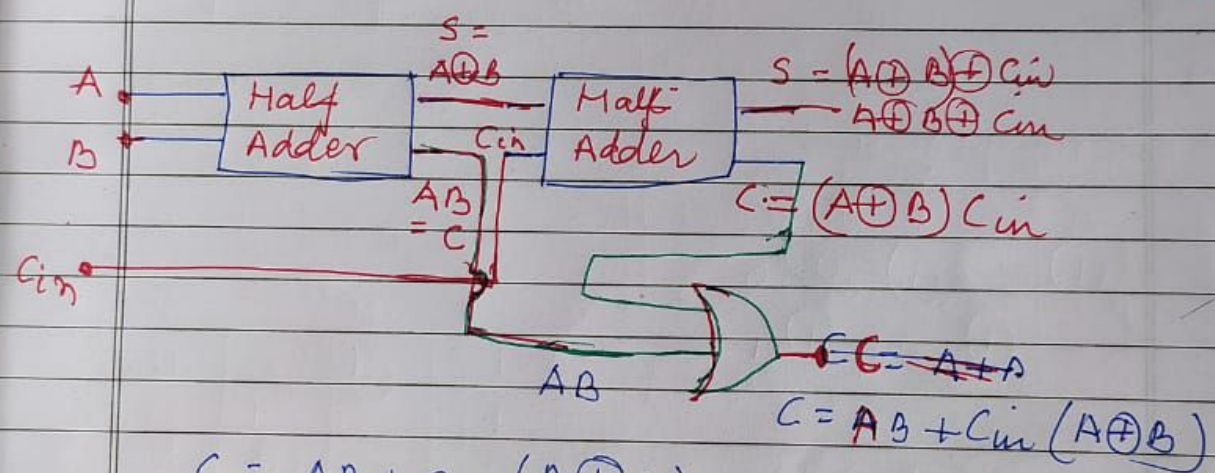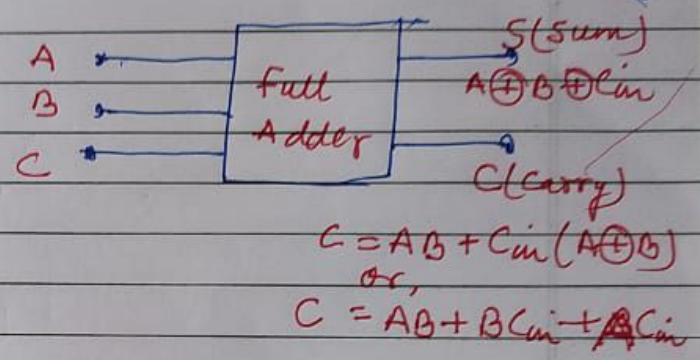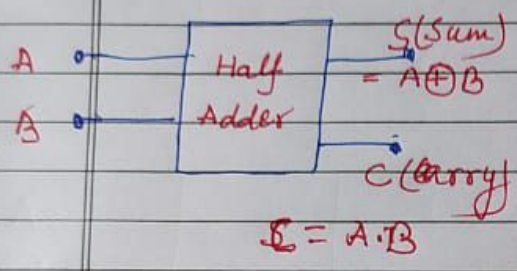

$$\begin{aligned}
 C &= AB + C_{in}(A \oplus B) \\
 &= AB + C_{in}(A\bar{B} + \bar{A}B) \\
 &= AB + A\bar{B}C_{in} + \bar{A}BC_{in} \\
 &= A(B + \bar{B}C_{in}) + \bar{A}BC_{in} \\
 &= A(B + C_{in}) + \bar{A}BC_{in} \\
 &= AB + AC_{in} + \bar{A}BC_{in} \\
 &= AB + C_{in}(A + \bar{A}B) \\
 &= AB + C_{in}(A + B)
 \end{aligned}$$

$\therefore (A + \bar{A}B) = A + B$

$AB + AC_{in} + B \cdot C_{in}$