

## **UNIT-3 MPHYECC-5**

### **OP-AMP APPLICATIONS**

**Submitted by:**

**Dr. Gargi Tiwari**


**Dept. of Physics**

The electronic circuits, which perform arithmetic operations are known as **arithmetic circuits**. Using op-amps, we can build basic arithmetic circuits such as an **adder** and a **subtractor**. Here, you will learn about each of them in detail.
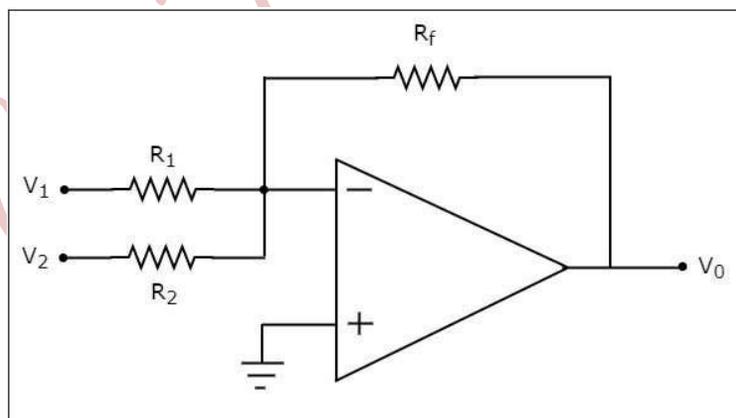
#### **Adder**

An adder is an electronic circuit that produces an output, which is equal to the sum of the applied inputs. This section discusses about the op-amp based adder circuit.

An op-amp based adder produces an output equal to the sum of the input voltages applied at its inverting terminal. It is also called as a summing amplifier, since the output is an amplified one. The circuit diagram of an op-amp based adder is shown in the following figure –



In the above circuit, the non-inverting input terminal of the op-amp is connected to ground. That means zero volts is applied at its non-inverting input terminal.

According to the virtual short concept, the voltage at the inverting input terminal of an op-amp is same as that of the voltage at its non-inverting input terminal. So, the voltage at the inverting input terminal of the op-amp will be zero volts.

The nodal equation at the inverting input terminal's node is

$$\frac{0 - V_i}{R_1} + \frac{0 - V_2}{R_2} + \frac{0 - V_0}{R_f} = 0$$

$$\Rightarrow \frac{V_1}{R_1} - \frac{V_2}{R_2} = \frac{V_0}{R_f}$$

$$V_0 = R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

If  $R_f=R_1=R_2=R$ , then the output voltage  $V_0$  will be –

$$V_0 = -R \left( \frac{V_1}{R} + \frac{V_2}{R} \right)$$


$$\Rightarrow V_0 = -(V_1 + V_2)$$

Therefore, the op-amp based adder circuit discussed above will produce the sum of the two input voltages  $V_1$  and  $V_2$ , as the output, when all the resistors present in the circuit are of same value. Note that the output voltage  $V_0$  of an adder circuit is having a negative sign, which indicates that **there exists a 180° phase difference between the input and the output.**
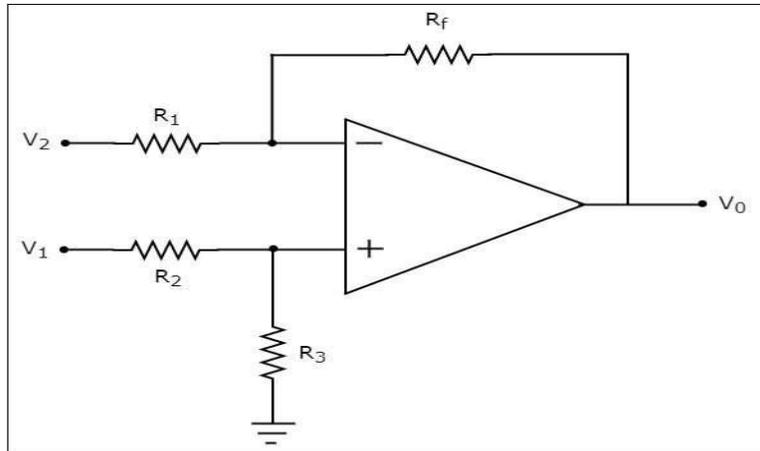
### **Subtractor**

A subtractor is an electronic circuit that produces an output, which is equal to the difference of the applied inputs. This section discusses about the op-amp based subtractor circuit. An op-amp based subtractor produces an output equal to the difference of the input voltages applied at its inverting and non-inverting terminals. It is also called as a difference amplifier, since the output is an amplified one.


The circuit diagram of an op-amp based subtractor is shown in the following figure –



Now, let us find the expression for output voltage  $V_0$  of the above circuit using superposition theorem using the following steps –
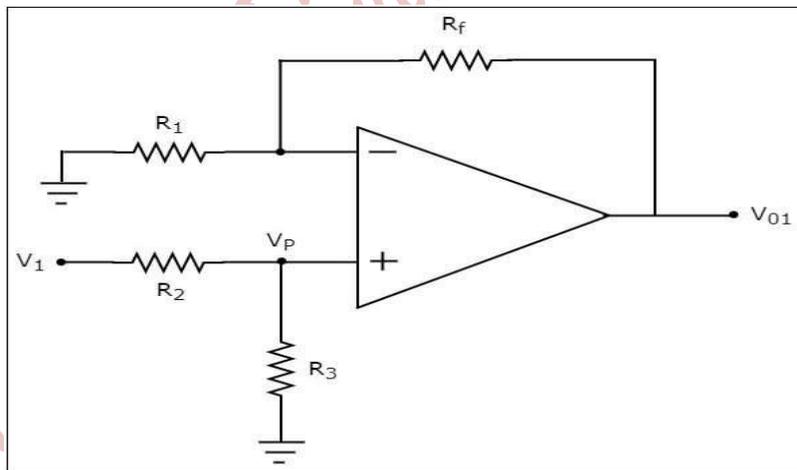
### Step 1

Firstly, let us calculate the output voltage  $V_{01}$  by considering only  $V_1$ . For this, eliminate  $V_2$  by making it short circuit. Then we obtain the modified circuit diagram as shown in the following figure –



Now, using the voltage division principle, calculate the voltage at the non-inverting input terminal of the op-amp.

$$\Rightarrow V_p = V_1 \left( \frac{R_3}{R_2 + R_3} \right)$$

Now, the above circuit looks like a non-inverting amplifier having input voltage  $V_p$ . Therefore, the output voltage  $V_{01}$  of above circuit will be


$$V_{01} = V_p \left( 1 + \frac{R_f}{R_1} \right)$$

Substitute, the value of  $V_p$  in above equation, we obtain the output voltage  $V_{01}$  by considering only  $V_1$ , as –

$$V_{01} = V_1 \left( \frac{R_2}{R_2 + R_3} \right) \left( 1 + \frac{R_f}{R_1} \right)$$
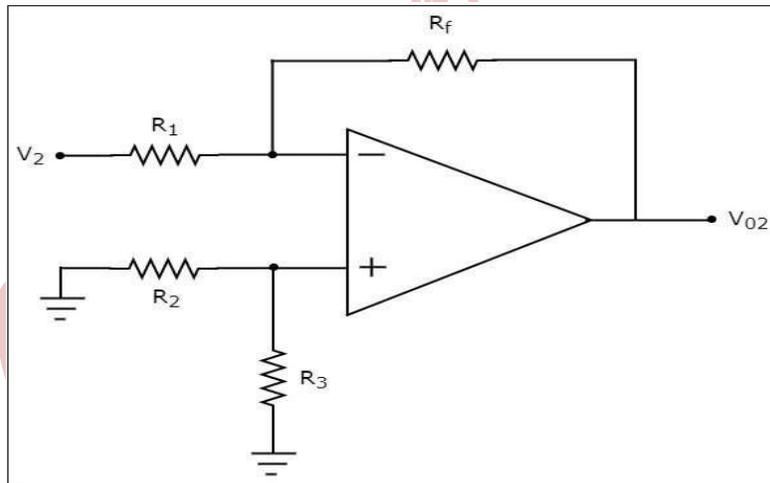
## Step 2

In this step, let us find the output voltage,  $V_{02}$  by considering only  $V_2$ . Similar to that in the above step, eliminate  $V_1$  by making it short circuit. The modified circuit diagram is shown in the following figure.



You can observe that the voltage at the non-inverting input terminal of the op-amp will be zero volts. It means, the above circuit is simply an inverting op-amp. Therefore, the output voltage  $V_{02}$  of above circuit will be –

$$V_{02} = -\left( \frac{R_f}{R_1} \right) V_2$$

### Step 3

In this step, we will obtain the output voltage  $V_0$  of the subtractor circuit by adding the output voltages obtained in Step1 and Step2. Mathematically, it can be written as

$$V_0 = V_{01} + V_{02}$$

Substituting the values of  $V_{01}$  and  $V_{02}$  in the above equation, we get –

$$V_0 = V_1 \left( \frac{R_3}{R_2 + R_3} \right) \left( 1 + \frac{R_f}{R_1} \right) + \left( -\frac{R_f}{R_1} \right) V_2$$
$$\Rightarrow V_0 = V_1 \left( \frac{R_3}{R_2 + R_3} \right) \left( 1 + \frac{R_f}{R_1} \right) - \left( \frac{R_f}{R_1} \right) V_2$$

If  $R_f = R_1 = R_2 = R_3 = R$ , then the output voltage  $V_0$  will be

$$\Rightarrow V_0 = V_1 \left( \frac{R}{R + R} \right) \left( 1 + \frac{R}{R} \right) - \left( \frac{R}{R} \right) V_2$$
$$\Rightarrow V_0 = V_1 \left( \frac{R}{2R} \right) (2) - (1)V_2$$
$$V_0 = V_1 - V_2$$

Thus, the op-amp based subtractor circuit discussed above will produce an output, which is the difference of two input voltages  $V_1$  and  $V_2$ , when all the resistors present in the circuit are of same value.